

Q1

Inputs			Outputs	
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

By K map we can derive equation

$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	3	1
A	1	5	1	6

for sum

$$= A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C}$$

$$S = A \oplus B \oplus C$$


$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	1	3
A	4	1	1	1

for carry


$$C = \bar{A}C + AB + BC$$

$$= AB + BC + CA$$

So nand equivalent of Xor gate is

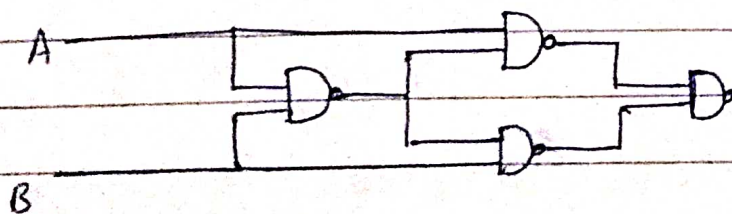

So, $A \oplus B \oplus C$

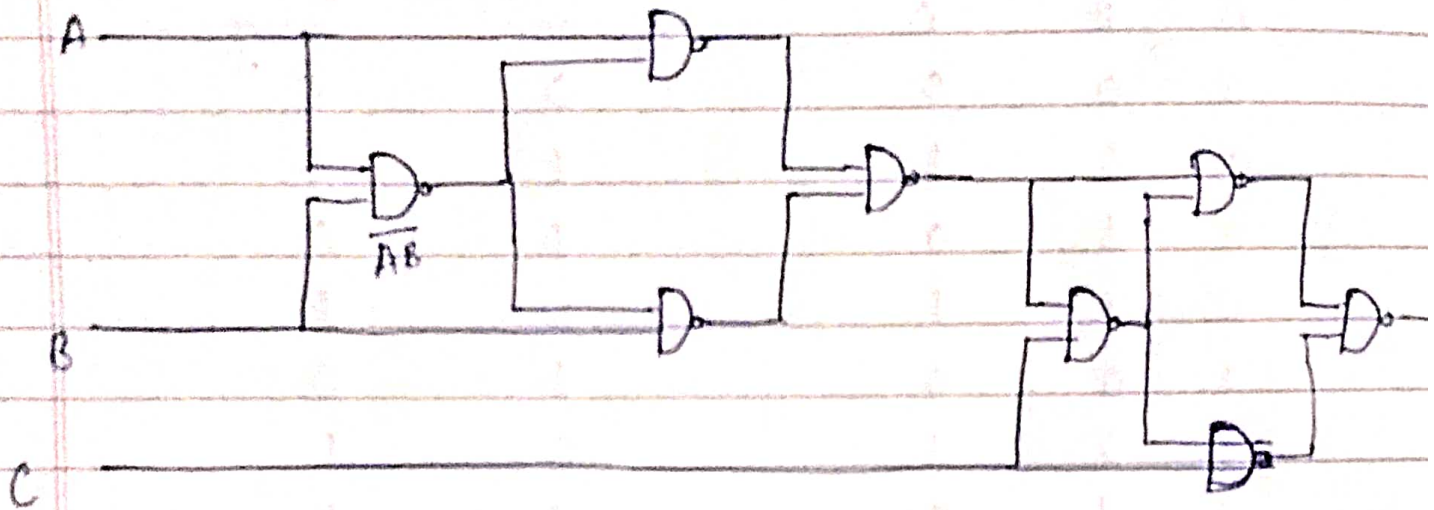


$$\text{Sum} = A \oplus B \oplus C$$

$$\begin{aligned} \text{Carry} &= AB + BC + CA \\ &= \overline{\overline{AB} + \overline{(A \oplus B)}} \end{aligned}$$

$$= \overline{\overline{AB} \cdot \overline{C(A \oplus B)}}$$

Both these terms are present in above circuit

So,

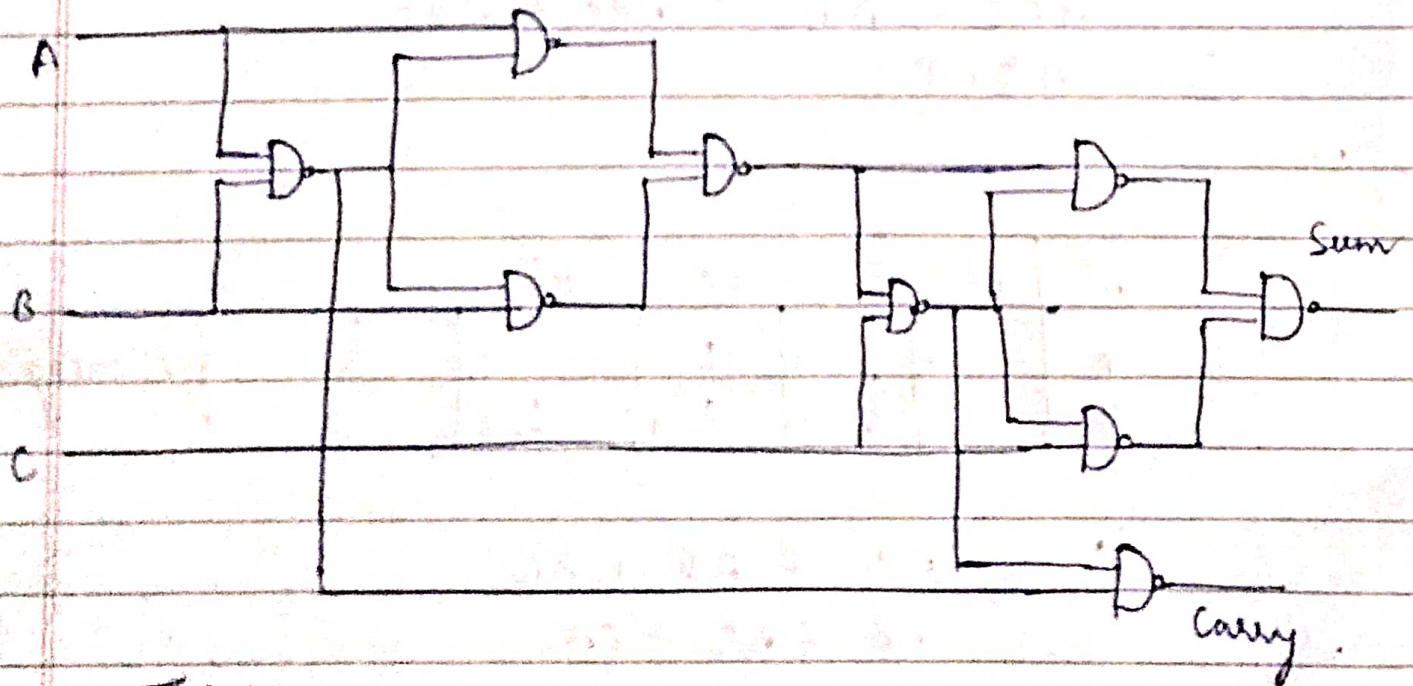

Total NAND gates required = 9

Q2

Input			Output	
A	B	Borrow(C) _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

A \ B	C			
	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	3	1
A	1	5	1	6

$$\text{Diff} = A \oplus B \oplus B_{in}$$

Let $X = A \oplus B$
by NOR gate

